

Name :

Roll No. :

Invigilator's Signature :



CS/BCA/SEM-1/BCA-101/2009-10

2009

DIGITAL ELECTRONICS

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

GROUP - A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for the following :

$10 \times 1 = 10$

- i) A 3-bit synchronous counter uses flip-flops with propagation delay time of 20 ns each. The maximum possible time required for change of state will be
 - a) 60 ns
 - b) 40 ns
 - c) 20 ns
 - d) none of these.
- ii) BCD subtraction is performed by using which complement representation ?
 - a) 1's
 - b) 2's
 - c) 10's
 - d) 9's.
- iii) The SOP form of logical expression is most suitable for designing logic circuits using only
 - a) XOR gates
 - b) NOR gates
 - c) NAND gates
 - d) OR gates.

- iv) The dual of a Boolean function is obtained by
- a) interchanging all 0s and 1s only
 - b) changing 0s to 1s only
 - c) changing 1s to 0s only
 - d) interchanging all 0s and 1s and '+' and '.' signs.
- v) When representing in the following code the consecutive decimal numbers differ only in one bit
- a) Excess-3
 - b) Gray
 - c) BCD
 - d) Hexadecimal.
- vi) In a $J - K$ flip-flop when $J = 1$ and $K = 1$ and clock = 1 the output will be
- a) toggle
 - b) 1
 - c) 0
 - d) recalls previous output.
- vii) $(AB + A'B + A'B)$ is equal to
- a) $A + B'$
 - b) $A' + B$
 - c) $A + B$
 - d) 1.
- viii) 2's complement of 1010101 is
- a) 0101011
 - b) 10101010
 - c) 1100000
 - d) 1000001.
- ix) The basic fuse technologies used in PROM are
- a) metal links
 - b) silicon links
 - c) $p-n$ junctions
 - d) all of these.
- x) In general, a boolean expression of $(n + 1)$ variable can be implemented using a multiplexer with
- a) 2^{n+1} inputs
 - b) 2^{n-1} inputs
 - c) 2^n inputs
 - d) None of these.

GROUP - B**(Short Answer Type Questions)**

Answer any *three* of the following. $3 \times 5 = 15$

2. Draw the neat diagram of 3-bits Bi-directional Shift Register using mode control (M). When M is logic zero then left shift and right shift for M is logic one.
3. Design 2-bit Gray-Binary converter using basic logic gates with proper truth table.
4. Draw the logic diagram and truth table of $J - K f/f$. Why is $J - K F/F$ much more versatile than $S - R F/F$?
5. What is a full subtractor ? Explain its basic structure with proper logic diagrams & truth tables. $1 + 4$
6. Realize the function $f(A, B, C) = \sum m(1, 3, 5, 6)$ by a multiplexer. Discuss the operation logic.

GROUP - C**(Long Answer Type Questions)**

Answer any *three* of the following. $3 \times 15 = 45$

7. a) Using K-map method minimize the following expression :

$$F(w, x, y, z) = m \sum (1, 5, 6, 12, 13, 14) + d \sum (2, 4).$$

8
- b) Implement Ex-OR gate using NAND Gate and NAND gate using NOR gate. $3 \frac{1}{2} + 3 \frac{1}{2}$
8. a) Design and implement Mod-6 synchronous counter considering lock out problem. Is the counter self-starting ? $8 + 1$
- b) Explain the difference between Ring and Johnson Counter with proper state diagram and circuit diagram. 6

9. a) Explain the concept of parity checking.
- b) Discuss about the design of an odd parity generator.
- c) What is biased exponent in relation to Floating Point Representation (FPR) ?
- d) Represent (- 1101011) in Floating Point Representation (FPR) for a 32-bit CPU. 3 + 4 + 3 + 5

10. What do you mean by race condition in flip-flop ? Design a *j - k* flip-flop and discuss its operation. Design and explain the functioning of the 4-bit adder-subtractor circuit.

3 + 5 + 7

11. Write short notes on any *three* of the following : 3 × 5

- a) Universal gates
- b) Decoder
- c) Shift Register
- d) Flip-flop excitation table
- e) Ripple counter.
-