





- xi) Full adder can add
- a) two binary numbers
  - b) three binary numbers
  - c) four binary numbers
  - d) none of these.
- xii) MOD - 10 counter can count up to
- a) 9
  - b) 10
  - c) 8
  - d) none of these.

**GROUP – B**

**( Short Answer Type Questions )**

Answer any *three* of the following.  $3 \times 5 = 15$

2. State and prove De-Morgan's theorems.
3. Express the Boolean function  $F = AB + \bar{A}C$  in a product of maxterm form.
4. Define multiplexer. Why is it called "Data Selector" ?  $3 + 2$
5. Use 4 : 1 MUX and other necessary logic gates to design a full adder.
6. What is flip-flop ? What is meant by race condition ?  $1 + 4$

**GROUP – C**

**( Long Answer Type Questions )**

Answer any *three* of the following.  $3 \times 15 = 45$

7. a) Using K-map method, simplify the following Boolean function and obtain minimal SOP expression :  
 $Y = \sum m ( 0, 2, 3, 6, 7 ) + \sum d ( 8, 10, 11, 15 )$ .
- b) Implement the Boolean Function  $F = ( A, B, C, D ) = \sum m ( 0, 1, 3, 8, 9, 15 )$  using two 4 - to-1 multiplexer and one OR gate.
- c) Design a gray code to binary converter circuit of 5 bits.  
What is nibble ?  $5 + 5 + ( 4 + 1 )$

8. a) Design a half adder circuit using minimum number of 2-input NOR gates only. Write Down the truth table and Boolean functions also.
- b) Convert a  $D$  flip-flop to a J-K flip-flop. You can use additional circuiting if required.
- c) What is full subtractor ? Explain its basic structure with proper logic diagrams and truth tables. 5 + 5 + 5
9. a) Convert the following :
- i)  $(AC15)_{16} = (?)_{10}$
- ii)  $(1011001)_2 = (?)_{10}$
- b) Discuss about the design of an odd parity generator.
- c) Explain the concept of parity checking.
- d) What is the advantage of J-K flip-flop over SR flip-flop. 5 + 5 + 2 + 3
10. a) What is the difference between sequential and combinational circuit ?
- b) Describe the propagation delay of a flip-flop.
- c) Express the Boolean function  $F = AB + A'C$  in a product of maxterm form. 5 + 5 + 5
11. a) Draw a block diagram and write truth table of a  $D$  flip-flop.
- b) Compare asynchronous and synchronous counter.
- c) Use 4 to 1 MUX and other necessary logic gate to design a full adder. 5 + 5 + 5
12. Write short notes on any *three* of the following : 3 × 5
- a) EPROM
- b)  $D$  flip-flop
- c) Ripple counter
- d) Encoder
- e) 4-bit parallel Adder.

